


# Report


Diluna Adeesha Warnakulasuriya

April 3, 2019

# Chapter 1

## Theoretical Part

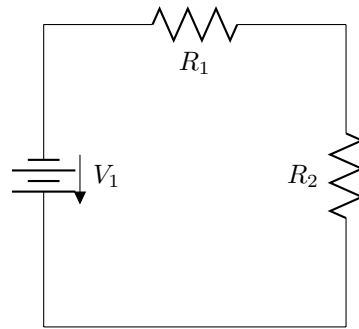

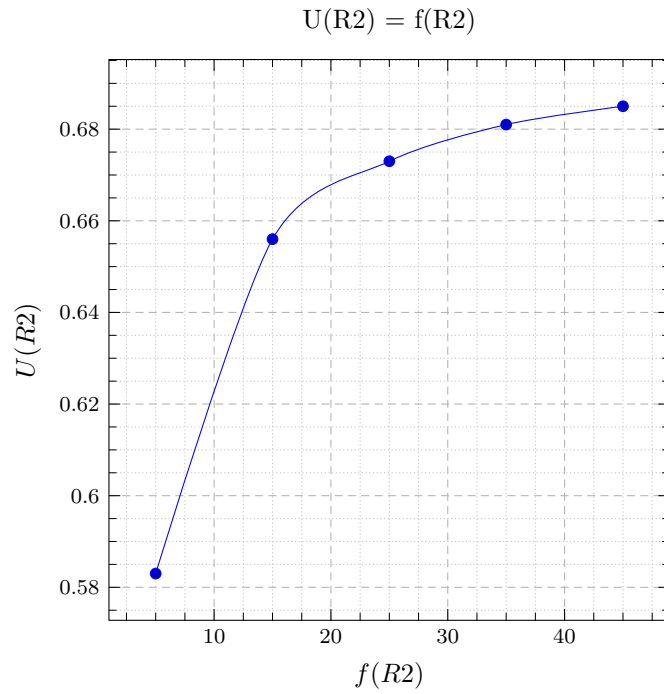

## 1.1 Circuit calculation

Calculated the Voltages on the Resistors  $R_1$  and  $R_2$  in DC circuit using Voltage Division Rule.

$$V_{R1} = (V_1 \times R_1) / (R_1 + R_2)$$

$$V_{R2} = (V_1 \times R_2) / (R_1 + R_2)$$

Variable	Value
$R_1$	1
$R_2$	1
$V_1$	0.7V
$V_{R2}$	0.35V
$V_{R1}$	0.35V


Figure 1.1: Table

## Chapter 2

# Practicle Part

### 2.1 Work with GEDA programs

#### 2.1.1 Work with gschem

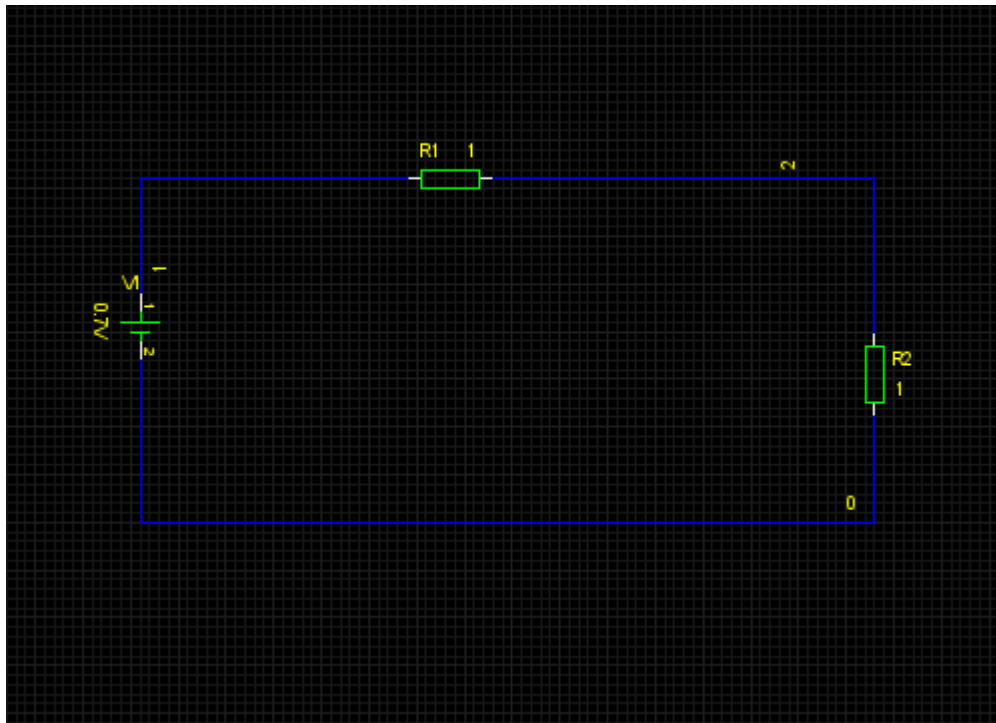

### 2.1.2 Work with gnetlist

\* Spice netlister for gnetlist V1 1 0 0.7V R2 0 2 1 R1 1 2 1 .END

### 2.1.3 Work with ngspice

This is the picture i got from plotting Connectin "1"

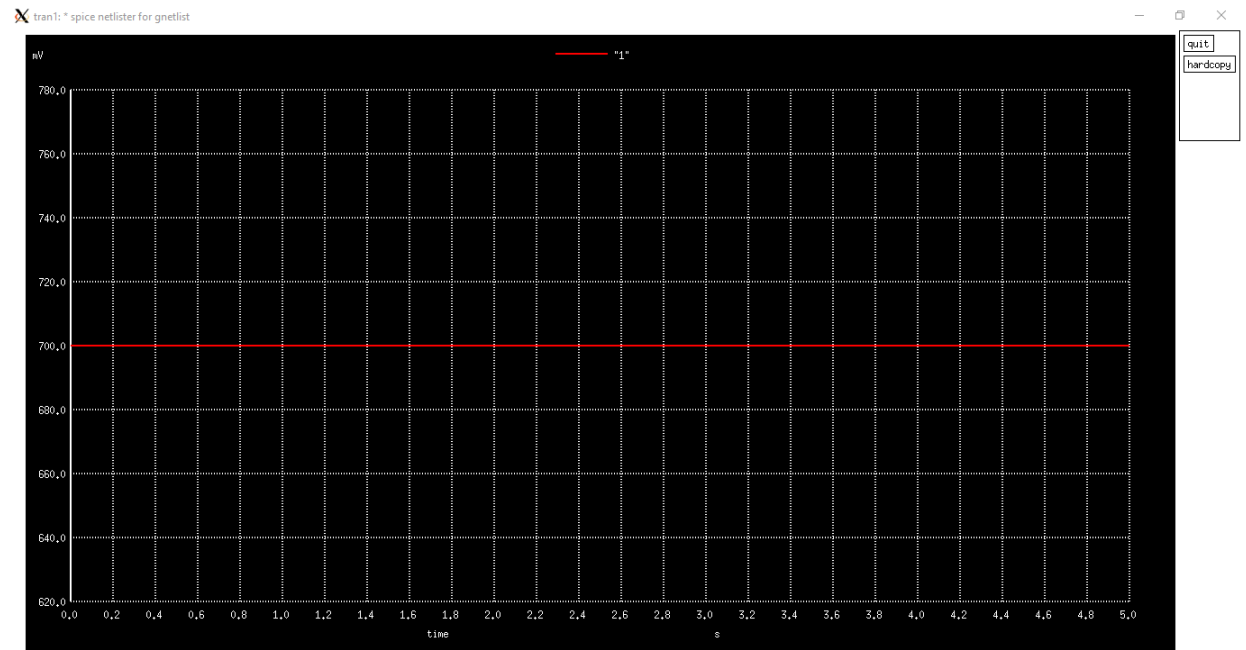


Figure 2.1: 011.png

This is the picture i got from plotting Connectin "2"

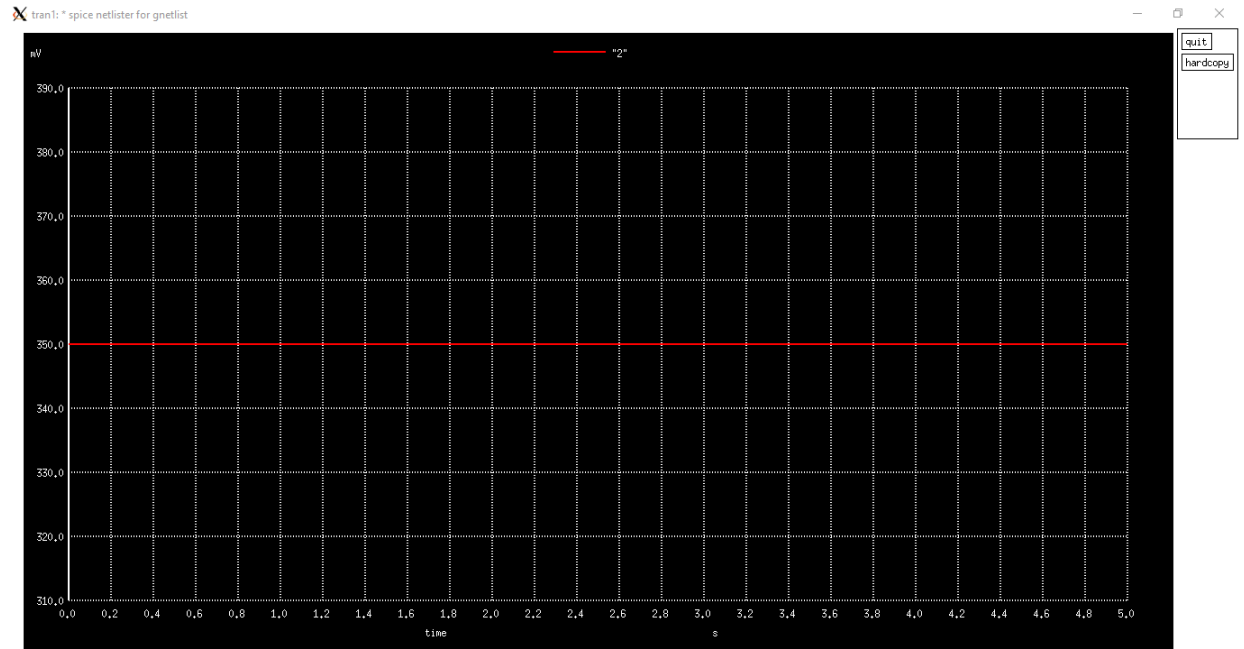


Figure 2.2: 012.png

## 2.2 work with QUCS programs

I setup a circuit with a graphical user interface (GUI) and simulate the DC signal and noise behaviour of the circuit. After that simulation has finished i viewed the simulation results on a presentation window.

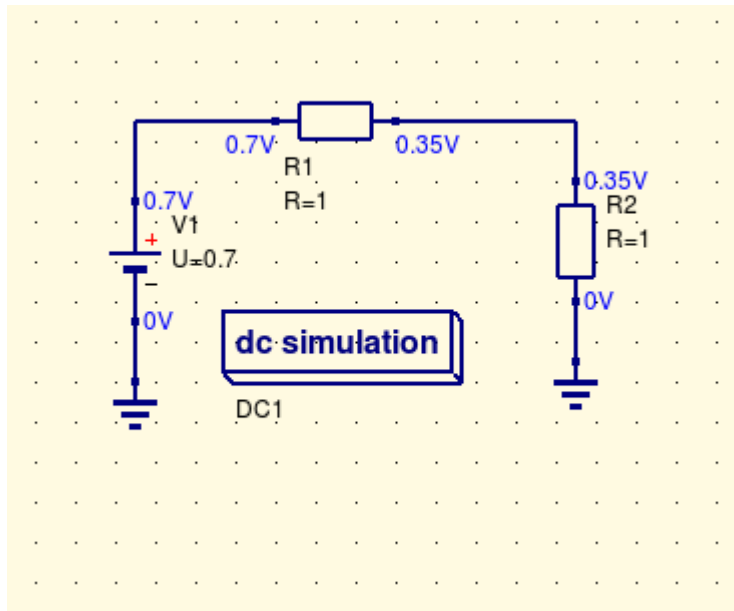


Figure 2.3: The QUCS schematics environment

- Perform elementary DC mode simulation with the F8 key, which results in calculations and determines the voltage on the resistor R2.
- It is shown in the image as 0.35V.
- The simulator variable that derives this value is designated R2.V.



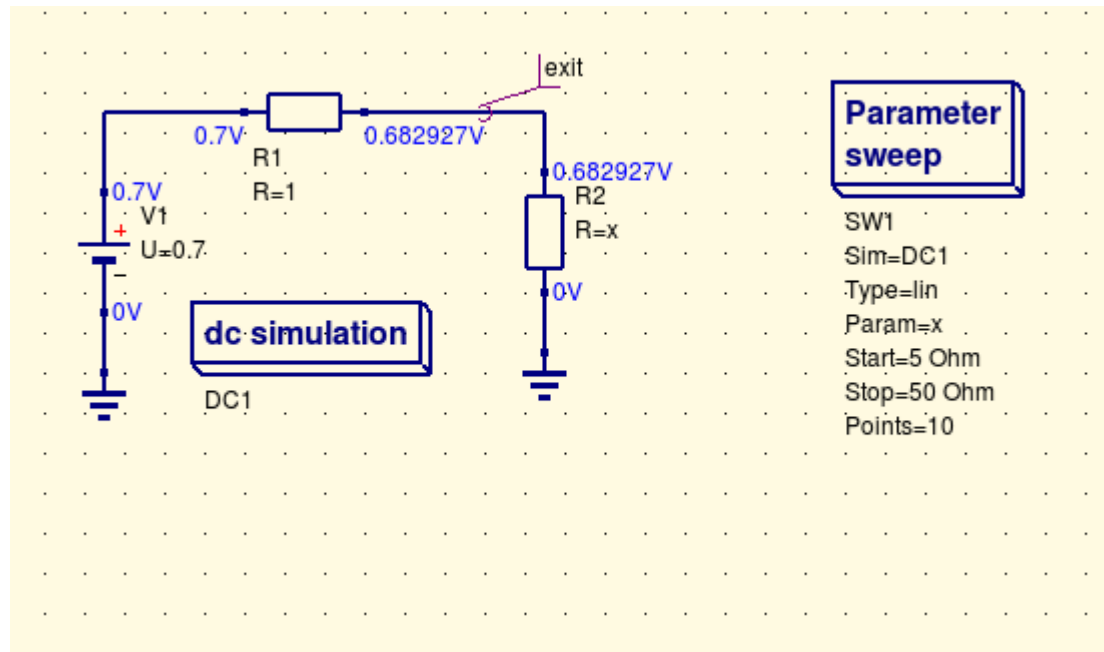


Figure 2.4: Parameter sweep mode

- the value of resistor  $R2$  to the symbol  $x$ , which will serve as the argument for the current circuit calculation.  
symbol:  $x$  has also written in the Param field of the component 'parameter sweep' attribute field.
- Changed the number of points to 10. simulating parameter  $x$  changed linearly
- value  $5\ \Omega$  to  $50\ \Omega$  at eleven points, where all the parameters of the circuit (current and voltages) calculated corresponding number of times because they depend on resistor  $R2$  value.
- the resulting parameter selection form, we can change them, obtain and estimate the calculated voltage value on the resistor  $R2$ -UR2

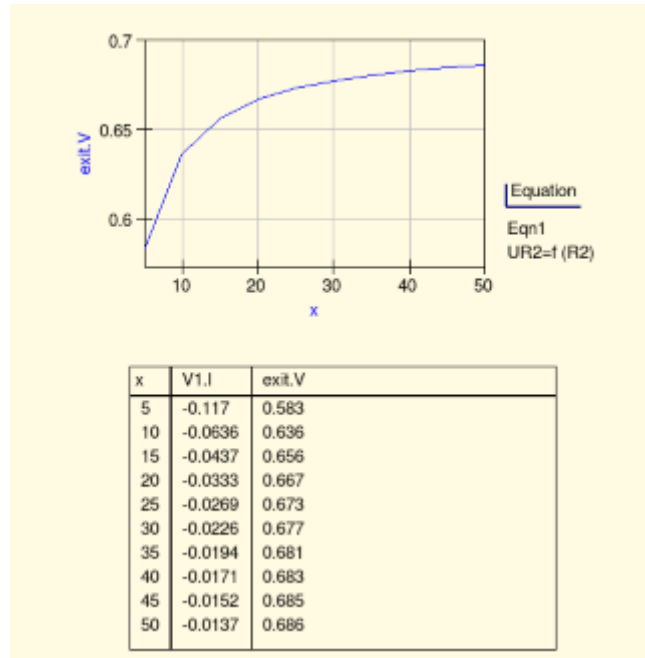


Figure 2.5: Curve and Table from Sweep simulation

- This graph showing the functional relationship between the value of R2 (which is variable) and the voltage on it - UR2. Generally it can be write as ' $UR2 = f(R2)$ '.
- The table display the current (V1.I) flowing through the voltage source V1 and the electrical circuit point with the signal output voltage (output V) against "Ground" as a function of parameter x.

## 2.3 References

- gschem to pcb tutorial, by Bill Wilson (release notes).
- gschem warmup, by Bill Willson.
- Mustafa Baser, “Effects of Conceptual Change and Traditional Confirmatory Simulations on Pre-Service Teachers’ Understanding of Direct Current Circuits”, Journal of Science Education and Technology, vol. 15, no. 5-6, Dec. 2006. Link: <http://dx.doi.org/10.1007/s10956-006-9025-3>.